

Digital Logic Circuits

'Common Combinational Circuits'

ELEC2200
Summer 2009

David J. Broderick
brodedj@auburn.edu
<http://www.auburn.edu/~brodedj>
Office: Broun 360



Modular Design

- Common combinational circuits are often lumped together into components
- A collection of gates is described by a block with inputs and outputs
- The behavior of the block is defined to meet a common purpose
- Used to make common operations easier/faster to implement



Adders

- We can use a combinational circuit to add binary values
- Recall:

Carries-->

1	1	1	0	0
	1	0	1	0
	1	1	1	1
	1	0	0	1

<--Result



Adders

- Each column can be thought of as a group of circuits
- Look at **inputs** and **outputs**

Carries-->

1	1	1	0	0
	1	0	1	0
	1	1	1	1
	1	0	0	1

<--Result



Adders

- Each column shares these set of inputs
- Look at **inputs** and **outputs**

Carries-->

1	1	1	0	0
	1	0	1	0
	1	1	1	1
	1	0	0	1

<--Result



Adders

- Each column shares these set of inputs
- Look at **inputs** and **outputs**

Carries-->

1	1	1	0	0
	1	0	1	0
	1	1	1	1
	1	0	0	1

<--Result



Adders

- Each column shares these set of inputs
- Look at **inputs** and **outputs**

Carries-->

1	1	1	0	0
	1	0	1	0
	1	1	1	1
	1	0	0	1


<--Result



Half-Adder

- Ignoring carry-in:

c	a	b	s	c
	0	0	0	0
+	0	1	1	0
	1	0	1	0
	1	1	0	1

 

- $s = a(+)b$
- $c = a \cdot b$



Full-Adder

- With carry-in:

co	ci	a	b	ci	s	co	s				
0	0	0	0	0	0	0	a\b ci	00	01	11	10
0	a	0	0	1	1	0	0	0	1	0	1
+	b	0	1	0	1	0	1	1	0	1	0
	s	0	1	1	0	1	co				
		1	0	0	1	0	a\b ci	00	01	11	10
		1	0	1	0	1	0	0	0	1	0
		1	1	0	0	1	1	0	1	1	1
		1	1	1	1	1					

- $s = a(+)b$
- $c = a \cdot b$




Full-Adder

- $s = a \cdot \bar{b} \cdot \bar{c}_i + \bar{a} \cdot b \cdot \bar{c}_i + a \cdot b \cdot c_i + \bar{a} \cdot \bar{b} \cdot c_i$

$$s = a(+)b(+)c_i$$

 - $c_o = a \cdot c_i + b \cdot c_i + a \cdot b$



S

a\b c_i	00	01	11	10
0	0	1	0	1
1	1	0	1	0


CO

a\b c_i	00	01	11	10
0	0	0	1	0
1	0	1	1	1




Ripple-Carry Adder

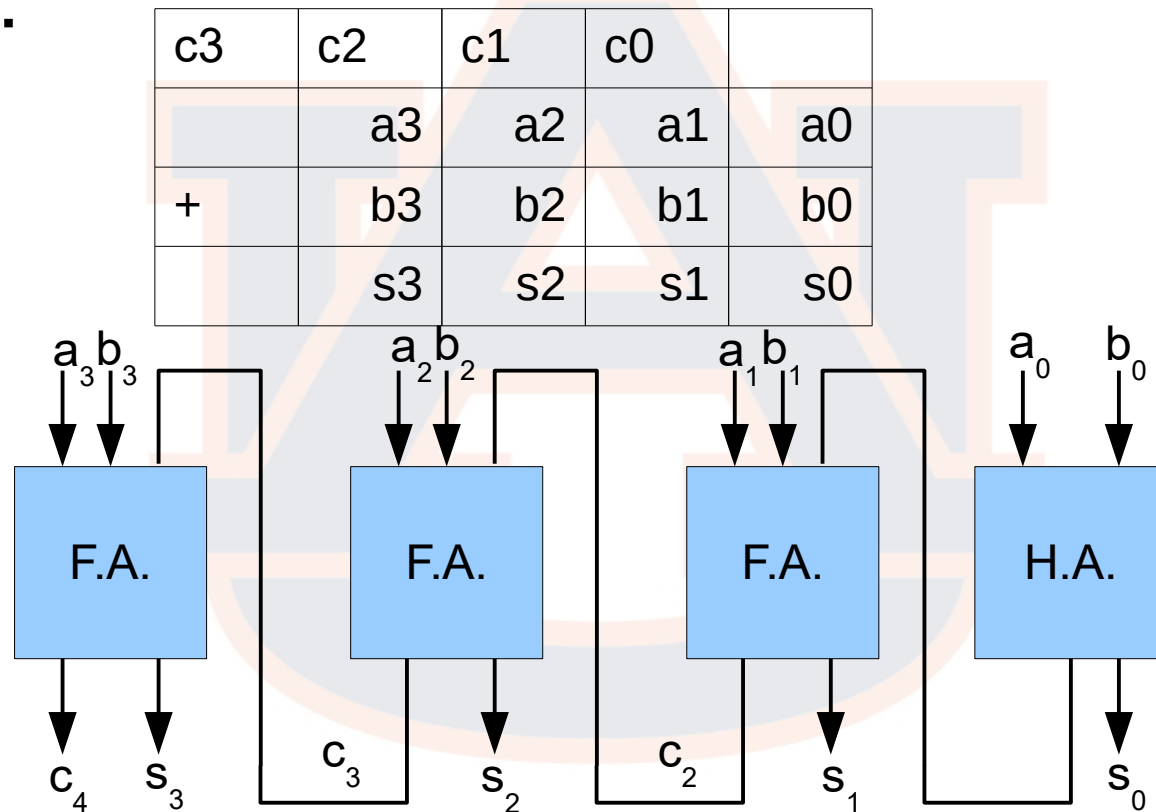- A slow (but small) method of adding larger values:



Ripple-Carry Adder

- Often redrawn as:

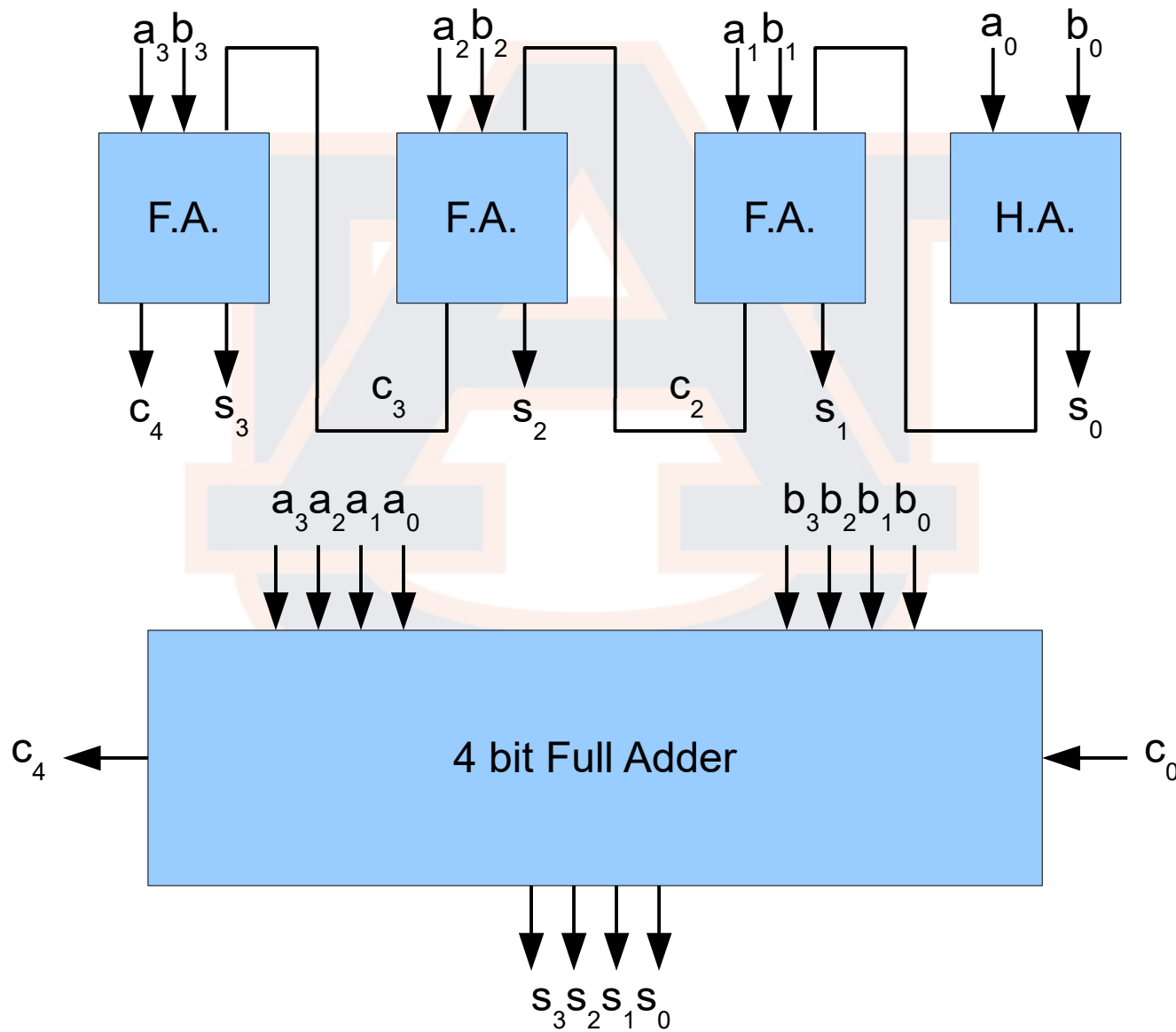


Fully Parallel Adders

- If all inputs are known (9 inputs) expressions can be written for all outputs (5 outputs)
- Creates a faster adder but does not scale well
 - 9 input K-map!
- Intermediate solutions exist
 - Carry look-ahead adders
 - Carry-save adders
 - etc...




Subtractors

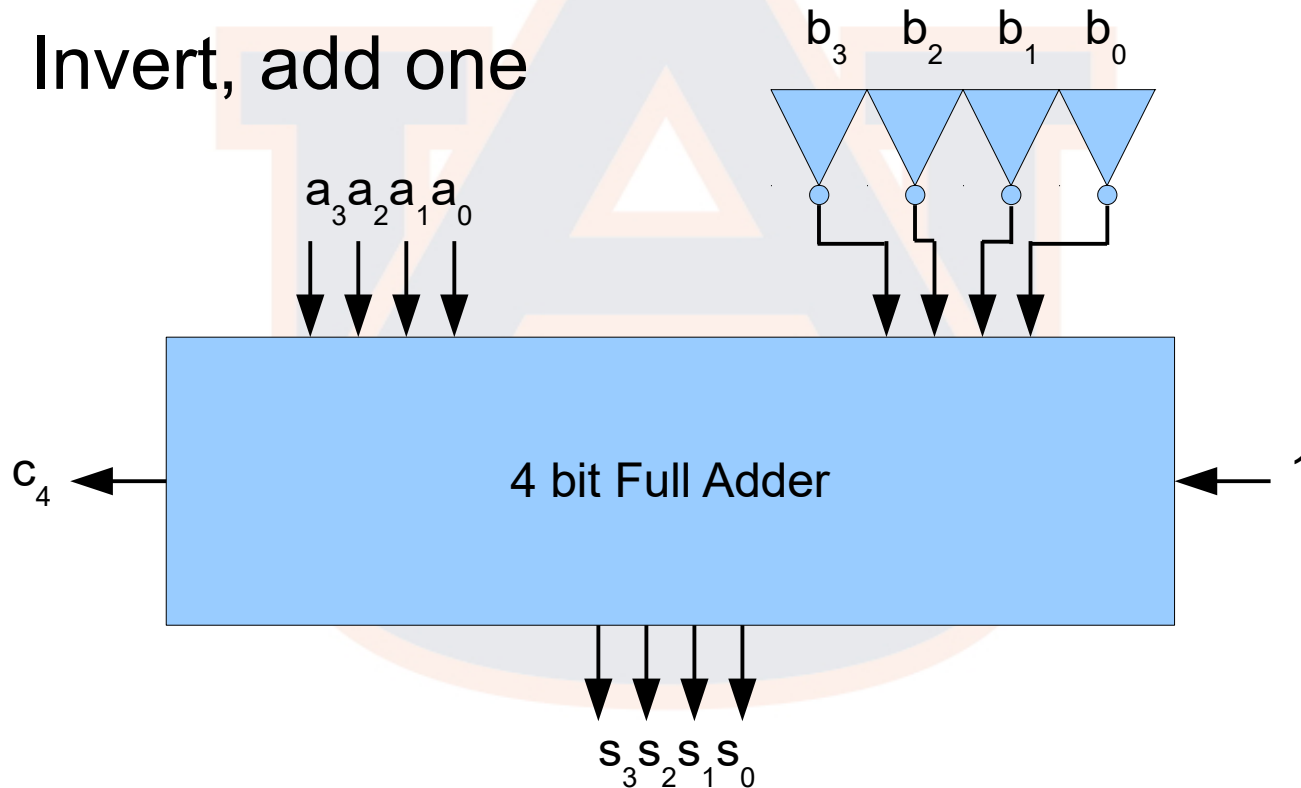- Using 2's complement, subtraction looks like addition
 - Invert, add one




Multiplexers

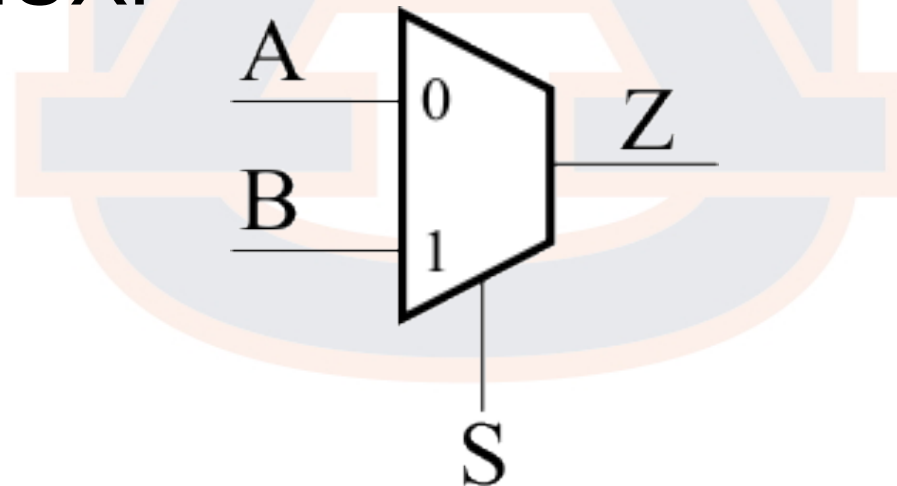- Selects between multiple inputs to pass through to output
- n control signals are used to select up to 2^n inputs to pass to the single output
- A 2-to-1 MUX:



Multiplexers

 
- If $S=0$, $Z=A$
- If $S=1$, $Z=B$
- 3 inputs, 1 output



A	B	S	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


AB\S	0	1
00	0	0
01	0	1
11	1	1
10	1	0

$$Z = A \cdot \bar{S} + B \cdot S$$

 

Multiplexers

 - The multiplexer is a functionally complete set
- Need to show AND, OR, and NOT
- AND: $A=0$, $Z=B \cdot S$




A	B	S	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



Multiplexers

 - The multiplexer is a functionally complete set
- Need to show AND, OR, and NOT
- OR: $B=1, Z=A+S$




A	B	S	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



Multiplexers

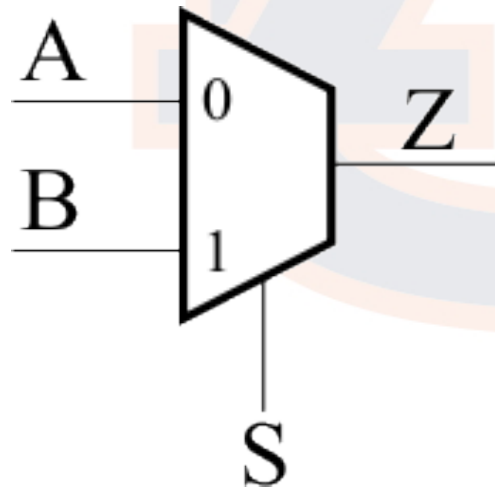- The multiplexer is a functionally complete set
- Need to show AND, OR, and NOT
- NOT: $A=1, B=0, Z=\bar{S}$



A	B	S	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



Adder/Subtractor




Adder/Subtractor



Demultiplexers

 - Opposite of a multiplexer
- Input passed to selected output, all other outputs are zero




Decoders/Encoders

- Decoders
 - N inputs produce M outputs (typically $M > N$)
 - BCD to 7-segment decoder is a good example
- Encoder
 - N inputs produce M outputs (typically $N > M$)
 - We could just as easily have taken the 7-segment values, (A-G) and encode to BCD or HEX
- Convertors
 - N inputs produce M outputs (typically $N = M$)
 - Binary to Gray-Code convertor is a good example



Comparators

 - Equal-to comparators use XOR function
 - XOR produces 1 when inputs differ
 - Do bit-wise compare of N bit number
- Outputs of XORs then ORed together.
- If any bit differs, output = 1




Comparators

- Greater than/Less than performed with 2's comp subtraction
- Examine sign (MSB) of result to determine result



Parity Circuits

 - Parity makes use of the XOR function
 - XOR produces a 1 for an odd # of 1s
 - Implements even parity
 - An XNOR on the output can be used for odd parity



Parity Circuits

- Check for correct parity by comparing P_{gen} with incoming parity bit P_{in}
- One more XOR gate for comparison

